

# ECE 528


## Final Project Report

Shivam Kundan

Anup Kumar Biswas

## Design Description

The aim of this project was to design a simple 32-bit, 5-pipeline-stage MIPS CPU which can execute basic arithmetic and logical instructions. The design is implemented on a Basys-3 Board with Artix-7 FPGA.

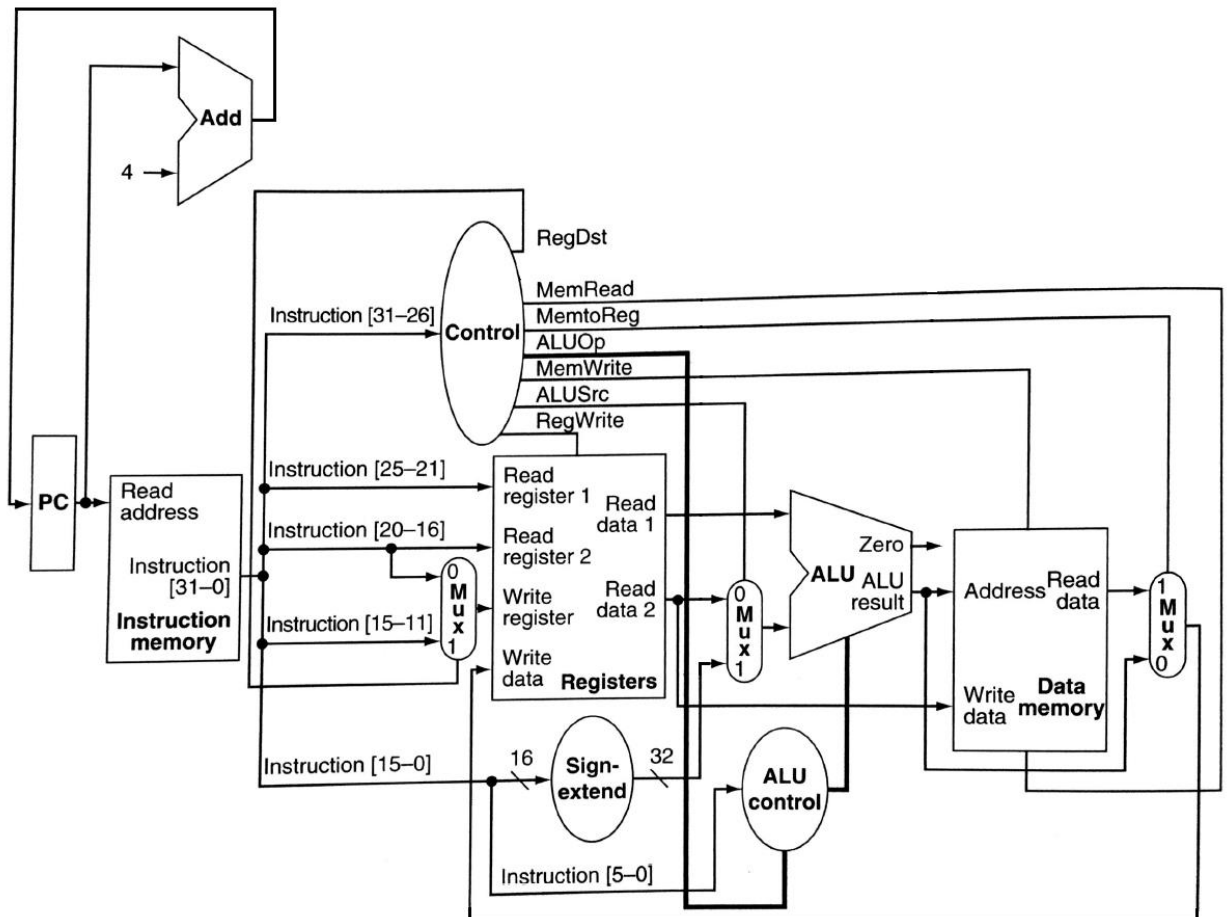

*Fig 1: Basic Representation of CPU*

The top-level design consists of five modules, corresponding to each stage of a 5-stage MIPS pipeline – IF, ID, EX, MEM, and WB.

## 1. Instruction Fetch Module

```

1. module IF_top(input clk,
2.               input en,
3.               input reset,
4.               output [31:0] IF_out
5.             );
6.
7.   wire [5:0] PC_out;
8.   PC PC0 (clk,reset,en,PC_out);
9.   wire [31:0] instruction;
10.
11.   Instruction_Memory_BROM Instruction_Memory(PC_out,clk,instruction);
12.
13.   Pipeline_Reg_Template IF_ID(clk,reset,instruction,IF_out);
14.
15. endmodule

```

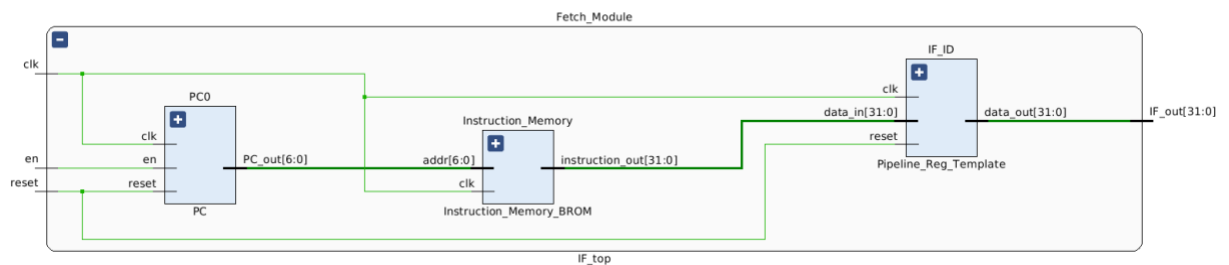


Fig 2: IF Top Module

### i. Program Counter

```

1. module PC(
2.   input clk,
3.   input reset,
4.   input en,
5.   output reg[6:0] PC_out); //Because we need 0 to 63
6.
7.   always @(posedge clk) begin
8.     if(reset)
9.       PC_out=63;
10.    else begin
11.      if(en) begin
12.        if (PC_out==63)
13.          PC_out=0;
14.        else
15.          PC_out = PC_out + 1;
16.      end
17.    else


```

```

18.             PC_out=PC_out;
19.         end
20.     end
21. endmodule

```

ii. Instruction Memory (Block ROM IP)

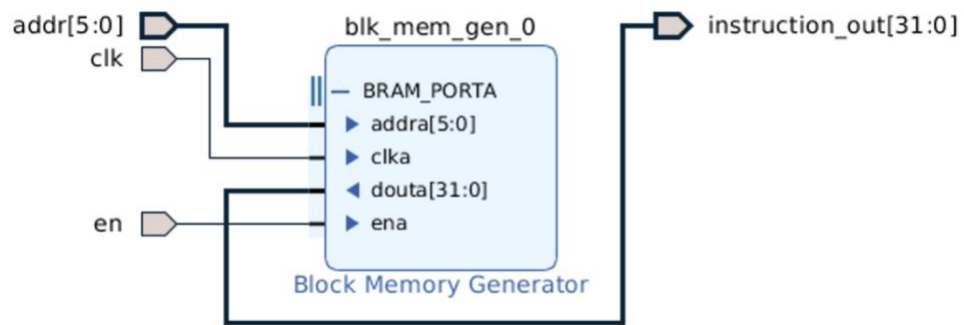

*Fig 3: IP Block Memory Design*

iii. IF/ID Pipeline Register

```

1. module Pipeline_Reg_Template(
2.     input clk,
3.     input reset,
4.     input [31:0] data_in,
5.     output reg [31:0] data_out
6. );
7.
8.     always@(posedge clk) begin
9.         if (reset)
10.             data_out=0;
11.         else
12.             data_out=data_in;
13.     end
14.
15. endmodule

```

## 2. Decode Module

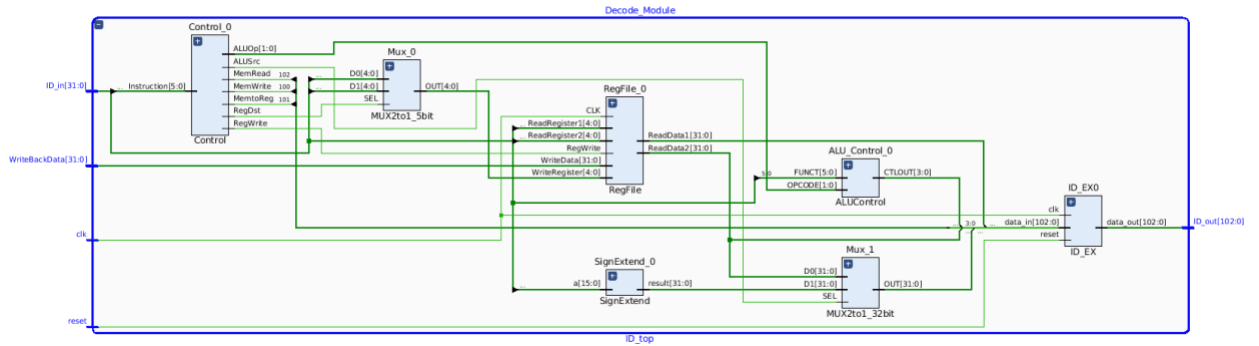


Fig 4: Decode Top Module

### i. Control Module

```


1. //MIPS decoder circuit plus ID_EX pipeline register
2.
3. module ID_top(input clk,
4.               input reset,
5.               input [31:0] ID_in,
6.               input [31:0] WriteBackData,
7.               output [102:0] ID_out
8.             );
9.
10.
11. //Internal connections
12. wire MemRead, MemtoReg, MemWrite, RegDst, ALUSrc, RegWrite;
13. wire [1:0] ALUOp;
14. wire [3:0] ALUct1OUT;
15. wire [4:0] WriteRegister;
16. wire [31:0] ReadData1, ReadData2, RegsWriteData, SignEOut, DataMemRead, RegFile_Out;
17. wire [7:0] PCOutWire;
18. reg en;
19.
20. //Instantiate Control Unit
21. Control Control_0(ID_in[31:26],
22.                  ALUOp,
23.                  MemRead,
24.                  MemWrite,
25.                  MemtoReg,
26.                  RegDst,
27.                  RegWrite,
28.                  ALUSrc
29.                );
30.
31. //Instantiate Register File
32. RegFile RegFile_0(clk,
33.                   RegWrite,
34.                   ID_in[25:21],
35.                   ID_in[20:16],
36.                   WriteRegister,
37.                   WriteBackData,

```

```

38.         ReadData1,
39.         ReadData2
40.     );
41.
42.     //Instantiate ALU Control
43.     ALUControl ALU_Control_0(ID_in[5:0],
44.                               ALUOp,
45.                               ALUctlOUT
46.     );
47.     //Instantiate Sign Extend Module
48.     SignExtend SignExtend_0(ID_in[15:0],
49.                               SignEOut
50.     );
51.     //Instantiate mux0
52.     MUX2to1_5bit Mux_0(ID_in[20:16],
53.                         ID_in[15:11],
54.                         WriteRegister,
55.                         RegDst
56.     );
57.
58.     //Instantiate mux1
59.     MUX2to1_32bit Mux_1(ReadData2,
60.                         SignEOut,
61.                         RegFile_Out,
62.                         ALUSrc
63.     );
64.
65.     //Assign output values
66.     wire [102:0] dout_temp;
67.     assign dout_temp[102]=MemRead;
68.     assign dout_temp[101]=MemtoReg;
69.     assign dout_temp[100]=MemWrite;
70.     assign dout_temp[99:68]=ReadData1;
71.     assign dout_temp[67:36]=RegFile_Out;
72.     assign dout_temp[35:4]=ReadData2;
73.     assign dout_temp[3:0]=ALUctlOUT;
74.
75.     //Instantiate ID_EX pipeline register
76.     ID_EX ID_EX0(clk,reset,dout_temp,ID_out);
77.
78. endmodule

```

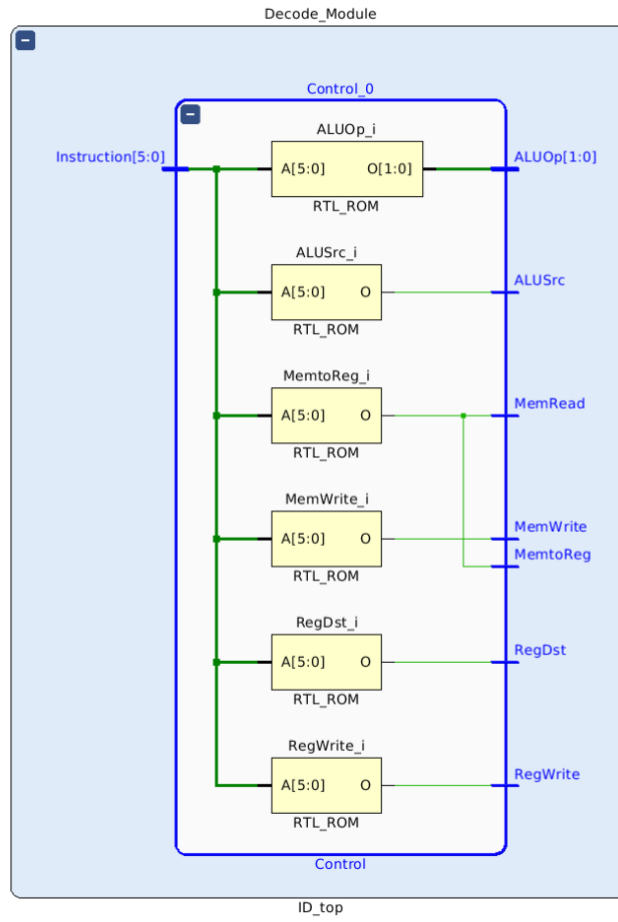

*Fig 5: Control Signals Module*

ii. Register File (32-bit\*32-bit)

```
1. /*This module implements a 32x32-bit MIPS register file.*/
2.
3. module RegFile(input CLK,
4.                 input RegWrite,
5.                 input [4:0] ReadRegister1,
6.                 input [4:0] ReadRegister2,
7.                 input [4:0] WriteRegister,
8.                 input [31:0] WriteData,
9.                 output [31:0] ReadData1,
10.                output [31:0] ReadData2
11.                )
12. reg [31:0] Regist [31:0]; //Internal registers
13. integer i; //Used for initializing
14.
15. //All registers contain 0 initially (Only for Simulation)
16. initial
17.     begin
18.         for(i = 0; i < 32; i = i + 1)
19.             Regist[i] = 32'b0;
20.     end
21.
22. always @(posedge CLK)
23.     if (RegWrite) Regist[WriteRegister] = WriteData; //Write
        operation
24.     assign ReadData1 = ReadRegister1 ? Regist[ReadRegister1]:0; //Read oper
        ation
25.     assign ReadData2 = ReadRegister2 ? Regist[ReadRegister2]:0; //Read oper
        ation
26.
27. endmodule
```

iii. ALU Control Module


```
1. /*This file implements a MIPS ALU control module.*/
2.
3. module ALUControl(input wire [5:0] FUNCT,
4.                   input wire [1:0] OPCODE,
5.                   output reg [3:0] CTLOUT
6.                   );
7. reg [3:0] Function;
8.
9. always @(*)
10.     begin
11.         Function=0;
12.         case(FUNCT[3:0])
13.             4'b0000: Function = 4'b0010; //Add
14.             4'b0010: Function = 4'b0110; //Sub
15.             4'b0100: Function = 4'b0000; //And
16.             4'b0101: Function = 4'b0001; //Or
17.             4'b0110: Function = 4'b1101; //Nand
18.             4'b0111: Function = 4'b1100; //Nor
19.             4'b1010: Function = 4'b0111; //slt
20.             default: Function = 4'b0000;
21.         endcase
```



```

22.     end
23.
24. always@(*)
25.     begin
26.         case(OPCODE)
27.             4'b0000: CTLOUT = 4'b0010; //Add
28.             4'b0010: CTLOUT = Function;
29.             default: CTLOUT = 0;
30.         endcase
31.     end
32. endmodule

```

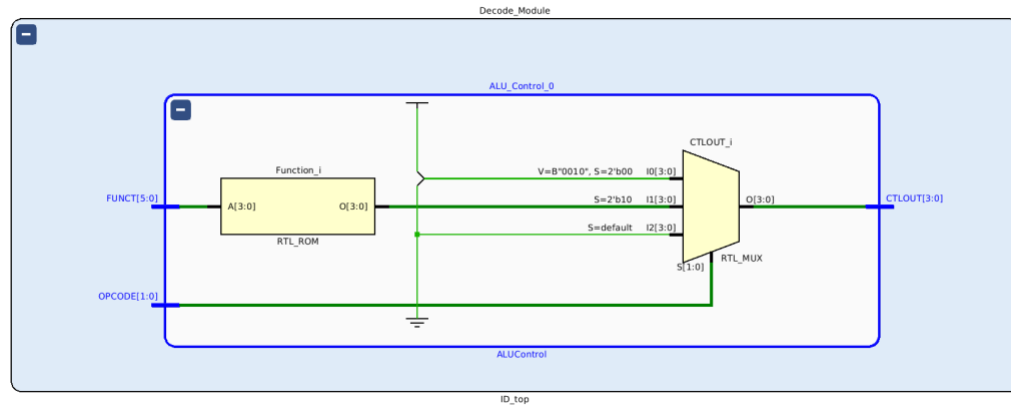

*Fig 6: ALU Control Module*

#### iv. Sign Extend Module

```

1. module SignExtend(input [15:0] a,
2.                   output [31:0] result);
3.
4. assign result = {{16{a[15]}}, {a[15:0]}};
5.
6. endmodule

```

#### v. 2-to-1 Multiplexer (5-bit)

```

1. module MUX2to1_5bit(D0, D1, OUT, SEL);
2.     input [4:0] D0, D1;
3.     input SEL;
4.     output [4:0] OUT;
5.     assign OUT = (SEL == 0) ? D0:D1;
6. endmodule

```

#### vi. 2-to-1 Multiplexer (32-bit)

```

1. module MUX2to1_32bit(D0, D1, OUT, SEL);
2.     input [31:0] D0, D1;

```

```
3.     input SEL;
4.     output [31:0] OUT;
5.     assign OUT = (SEL == 0) ? D0:D1;
6. endmodule
```

vii. ID/EX Pipeline Register

```
1. module ID_EX(
2.     input clk,
3.     input reset,
4.     input [102:0] data_in,
5.     output reg [102:0] data_out
6. );
7.
8.     always@(posedge clk) begin
9.         if (reset)
10.             data_out=0;
11.         else
12.             data_out=data_in;
13.         end
14.
15. endmodule
```

### 3. Execute Module

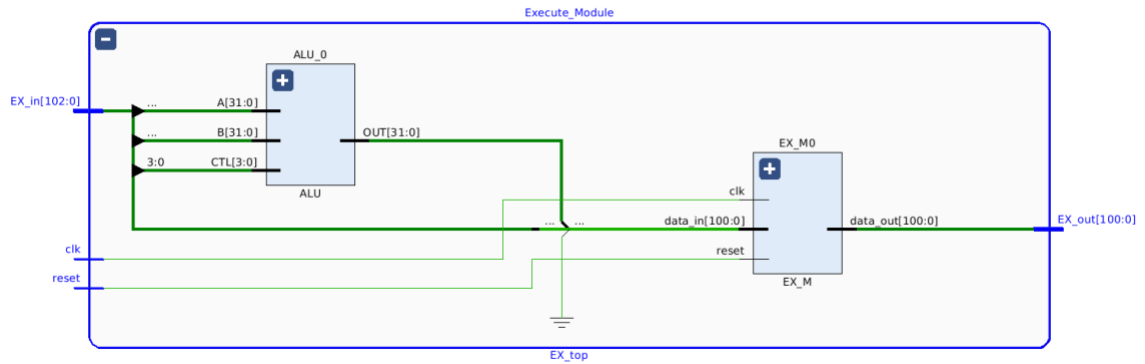


Fig 7: Execute Top Module

#### i. ALU

```

1.  /*This module implements an ALU.*/
2.
3.  module ALU(input [3:0] CTL,
4.             input [31:0] A,
5.             input [31:0] B,
6.             output reg [31:0] OUT
7.             );
8.
9.
10.     always @(*)
11.     begin
12.         case(CTL)
13.             4'b0000: OUT = A & B;           //And
14.             4'b0001: OUT = A | B;           //Or
15.             4'b0010: OUT = A + B;           //Add
16.             4'b0110: OUT = A - B;           //sub
17.             4'b0111: OUT = (A < B) ? 1:0;   //Set less than
18.             4'b1100: OUT = ~(A | B);        //Nor
19.             4'b1101: OUT = ~(A & B);        //Nand
20.             default: OUT = 0;
21.         endcase
22.     end
23. endmodule

```

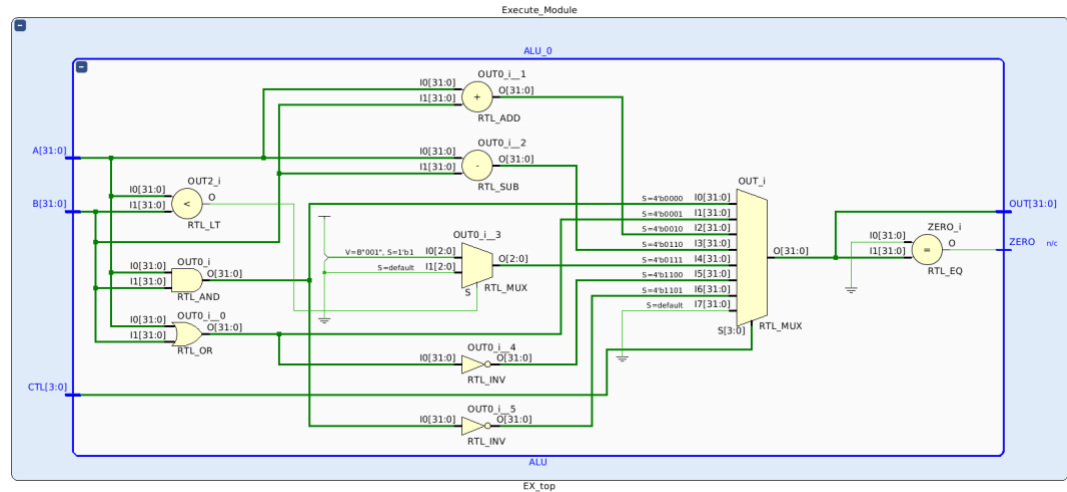


Fig 8: ALU Schematic

## ii. EX/MEM Pipeline Register

```

1. module EX_M(
2.     input clk,
3.     input reset,
4.     input [99:0] data_in,
5.     output reg [99:0] data_out
6. );
7.
8. always@(posedge clk) begin
9.     if (reset)
10.        data_out=0;
11.     else
12.        data_out=data_in;
13.     end
14.
15. endmodule

```

## 4. Memory Access Module

 


Fig 9: Memory Top Module

### i. Data Memory (256 addresses, 32-bits each)

```

1.  /*This file implements a MIPS data file.*/
2.
3.  module DataMemory(input wire CLK,
4.                    input wire [5:0] Address,
5.                    input wire rd,
6.                    input wire wr,
7.                    input wire [31:0] WriteData,
8.                    output wire [31:0] ReadData
9.                    );
10. reg [31:0] Mem [63:0]; //Internal registers
11. integer i;
12.     always @(posedge CLK)
13.     begin
14.         if(wr)
15.         begin
16.             Mem[Address] = WriteData;
17.         end
18.     end
19.
20.     assign ReadData = wr ? WriteData: Mem[Address][5:0];
21.
22. endmodule

```

### ii. MEM/WB Pipeline Register

```

1.  module MEM_WB(
2.      input clk,
3.      input reset,
4.      input [64:0] data_in,
5.      output reg [64:0] data_out
6.  );
7.
8.      always@(posedge clk) begin

```

```

9.     if (reset)
10.         data_out=0;
11.     else
12.         data_out=data_in;
13.     end
14.
15. endmodule

```

## 5. Write Back Module

 


Fig 10: Write Back Module

## User Constraints

```
1. ## Clock signal
2. #set_property PACKAGE_PIN W5 [get_ports clk]
3. #set_property IOSTANDARD LVCMOS33 [get_ports clk]
4. #create_clock -add -name sys_clk_pin -period 100000000.00 -
   waveform {0 500000000} [get_ports clk]
5.
6. ## Switches
7. set_property PACKAGE_PIN V17 [get_ports clk]                #Temporary clock
8. set_property IOSTANDARD LVCMOS33 [get_ports clk]
9. set_property PACKAGE_PIN T1 [get_ports en]
10. set_property IOSTANDARD LVCMOS33 [get_ports en]
11. set_property PACKAGE_PIN R2 [get_ports reset]
12. set_property IOSTANDARD LVCMOS33 [get_ports reset]
13.
14. ## LEDs
15. set_property PACKAGE_PIN V19 [get_ports dout[0]]
16. set_property IOSTANDARD LVCMOS33 [get_ports dout[0]]
17. set_property PACKAGE_PIN W18 [get_ports dout[1]]
18. set_property IOSTANDARD LVCMOS33 [get_ports dout[1]]
19. set_property PACKAGE_PIN U15 [get_ports dout[2]]
20. set_property IOSTANDARD LVCMOS33 [get_ports dout[2]]
21. set_property PACKAGE_PIN U14 [get_ports dout[3]]
22. set_property IOSTANDARD LVCMOS33 [get_ports dout[3]]
23. set_property PACKAGE_PIN V14 [get_ports dout[4]]
24. set_property IOSTANDARD LVCMOS33 [get_ports dout[4]]
25. set_property PACKAGE_PIN V13 [get_ports dout[5]]
26. set_property IOSTANDARD LVCMOS33 [get_ports dout[5]]
27. set_property PACKAGE_PIN V3 [get_ports dout[6]]
28. set_property IOSTANDARD LVCMOS33 [get_ports dout[6]]
29. set_property PACKAGE_PIN W3 [get_ports dout[7]]
30. set_property IOSTANDARD LVCMOS33 [get_ports dout[7]]
```

## Coefficient File

[illegible]

## Utilization Report

